

(3 Hours)

[Total Marks: 80]

- N.B.: (1) Question No. 1 is compulsory.  
 (2) Solve any **three** questions out of remaining **five**.  
 (3) Figures to **right** indicate **full marks**.  
 (4) Assume suitable data where **necessary**.

Q1. Solve any four

20

- Prove that NOR gate is a universal gate.
- Convert following decimal number to Binary, Octal, Hexadecimal and Gray code  
 $(2538)_{10}$
- Derive relation between  $\alpha$  and  $\beta$ .
- Design full adder using half adder and additional gates.
- Covert D flip flop to T flip flop.

Q2. a) Explain Voltage Divider Biasing Circuit with its stability factor.

10

b) Using Quine MC Cluskey Method determine Minimal SOP form for

10

$$F(A,B,C,D) = \sum m(0,1,3,7,8,9,11,15)$$

Q3. a) Implement following using only one 8:1 Multiplexer and few gates.

$$F(A,B,C,D) = \sum m(0,1,3,4,5,7,9,10,12,15)$$

10

b) With neat logic diagram explain operation of 4-bit Bidirectional Shift Register.

10

Q4. a) Design a Mod 12 asynchronous counter using J-K Flipflop.

10

b) Minimize the following four variable logic function using K-map

10

$$i) f(A,B,C,D) = \sum m(0,1,3,4,7,9,11,13,15)$$

$$ii) f(A,B,C,D) = \pi M(0,2,5,6,10,12,13,14)$$

Q5. a) Simplify following equation using Boolean algebra and Design using basic gates

10

$$i) (A+B)(A+C)$$

$$ii) (A+C)(AD+AD)+AC+C$$

b) Explain VHDL program format and write VHDL program for NAND gate.

10

Q6. Solve any four-

20

- 3-bit binary to Gray-code conversion.
- Working of Master slave J-K flip flop.
- Explain working Current Mirror Circuit.
- Write VHDL program for Half Subtractor circuit.
- Explain working of 3:8 Decoder.

84 LD

SE/IT/sem III/choice

33FB24E5AE4CF9DAE754A30C94281F7F

29/11/17.